

CSE 260 LAB ASSIGNMENT 5

~~105~~

NAME: ANIKA ISLAM

ID: 21101298

SECTION: 06

$$C = AB$$

$$S = A \oplus B$$

Group - 1

LAB - 5


A	B	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

~~Not~~

$$S = A \oplus B \oplus C$$

$$C = AB + (A \oplus B)C$$

x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

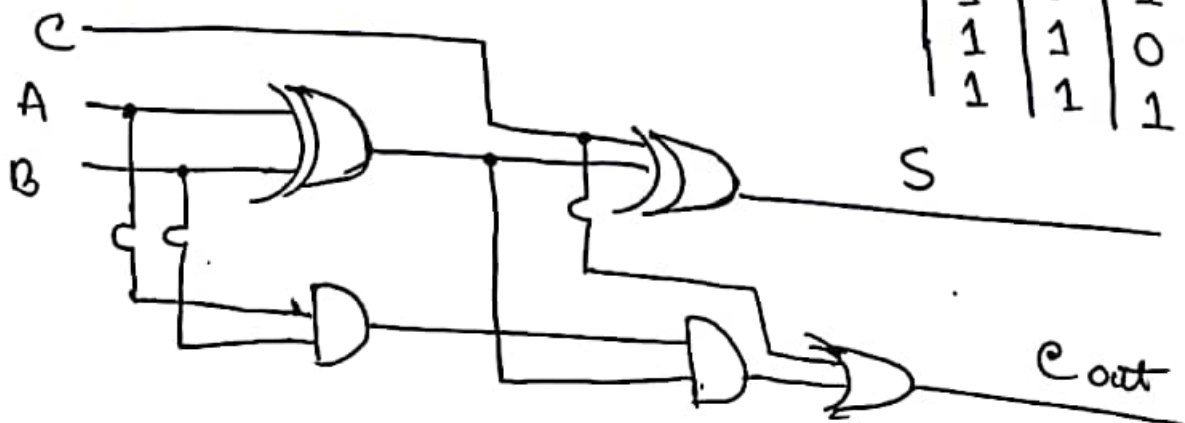~~Incomplete~~
~~Not~~

Lab Assignment 8

Report

(1) Name of Experiment: Design and implementation of 4-bit Parallel Binary Adder

(2) Objective:


- Obtain knowledge about the procedure behind addition in a digital device.
- Use ^{4 bit parallel} adder which can take upto 4 bits binary number.

(3) Required Components and Equipments:


- AND (IC - 7408)
- OR (IC - 7432)
- XOR (IC - 7486)
- 4 bit parallel adder (IC - 7483)
- Jumper wiring
- GND
- VCC (+5V)
- Switch
- Breadboard.
- Switch

(1) Experimental Setup (Circuit diagram)


Half adder:

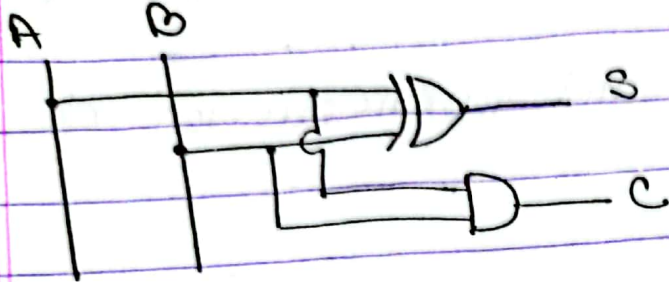

Full adder:

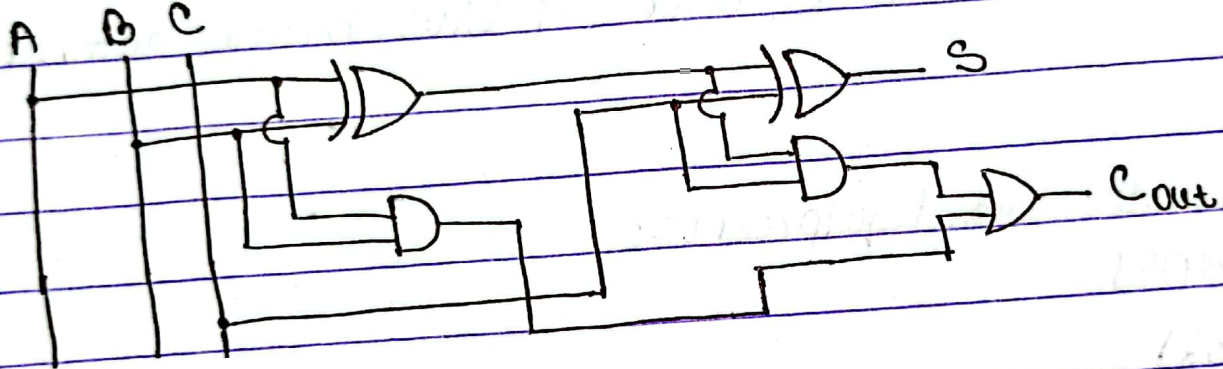

4 bit parallel adder:

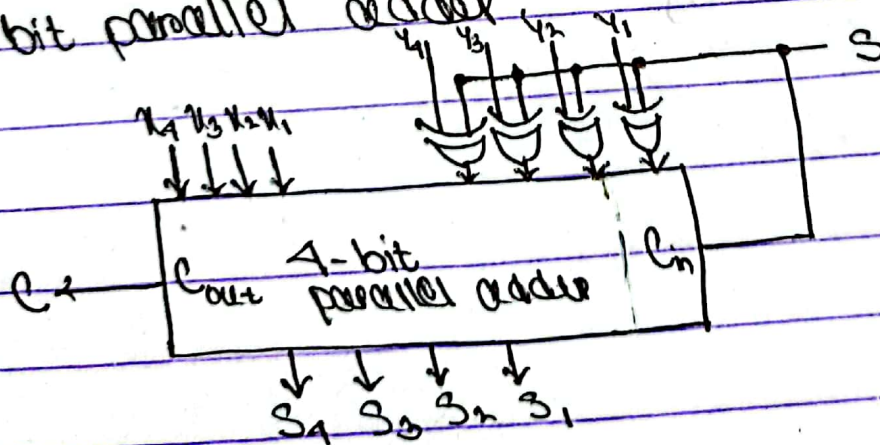

⑤ Results (Truth Tables) and Discussions (3rd questions) improvements / difficulties you faced etc.

Results:

half adder

A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$S = A'B + AB' = A \oplus B$$

$$C = AB$$

full adder

A	B	C	S	C _{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$S = A'B'C + A'BC' + AB'C' + ABC = A \oplus B \oplus C$$

$$C_{out} = A'BC + AB'C + ABC' + ABC = C(A \oplus B) + AB$$

Discussions

- Short circuit occurs due to loose connections of wiring or defect in ICs. ~~So we have to check the~~
- If wires and ICs are not checked before ~~making~~ building the circuit, any faults or damage in them ~~may~~ occurs in inaccurate output.