

Chapter 3 Notes | Digital Logic Design | Logic Gates & Boolean Algebra



Logic Gates

- The most basic digital devices are called gates.
- A gate has one or more inputs and produces an output that is a function of the current input values.
- The relationship between the input and the output is based on a **certain logic**

All Logic Gates

- NOT
- AND
- OR
- XOR
- XNOR
- NAND
- NOR

Truth Table

- Provides a listing of every possible combination of inputs and its corresponding outputs.

Basic Gates:

- AND, OR & NOT

Universal Gates:

- A **universal gate** is a **gate** which can implement any other **gate**
- NAND & NOR

NOT



INPUT		OUTPUT
A		
0		1
1		0

AND



INPUT		OUTPUT
A	B	
0	0	0
1	0	0
0	1	0
1	1	1

OR



INPUT		OUTPUT
A	B	
0	0	0
1	0	1
0	1	1
1	1	1

XOR



INPUT		OUTPUT
A	B	
0	0	0
1	0	1
0	1	1
1	1	0

NAND



INPUT		OUTPUT
A	B	
0	0	1
1	0	1
0	1	1
1	1	0

NOR



INPUT		OUTPUT
A	B	
0	0	1
1	0	0
0	1	0
1	1	0

XNOR



INPUT		OUTPUT
A	B	
0	0	1
1	0	0
0	1	0
1	1	1

Boolean Algebra

- Like any other deductive mathematical system, defined with a set of elements, a set of operators and a number of axioms or postulates.
- In Boolean algebra, set consists at least 2 variables say x & y , with 2 binary operations $\{+\}$ and $\{.\}$ and 1 unary operation $\{\prime\}$

Boolean Theorems & Postulates:

TABLE 2-1
Postulates and Theorems of Boolean Algebra

Postulate 2	(a) $x + 0 = x$	(b) $x \cdot 1 = x$
Postulate 5	(a) $x + x' = 1$	(b) $x \cdot x' = 0$
Theorem 1	(a) $x + x = x$	(b) $x \cdot x = x$
Theorem 2	(a) $x + 1 = 1$	(b) $x \cdot 0 = 0$
Theorem 3, involution	$(x')' = x$	
Postulate 3, commutative	(a) $x + y = y + x$	(b) $xy = yx$
Theorem 4, associative	(a) $x + (y + z) = (x + y) + z$	(b) $x(yz) = (xy)z$
Postulate 4, distributive	(a) $x(y + z) = xy + xz$	(b) $x + yz = (x + y)(x + z)$
Theorem 5, DeMorgan	(a) $(x + y)' = x'y'$	(b) $(xy)' = x' + y'$
Theorem 6, absorption	(a) $x + xy = x$	(b) $x(x + y) = x$

Duality

- Duality Principle** – every valid Boolean expression (equality) remains valid if the operators and identity elements are interchanged, as follows:

$$+ \leftrightarrow .$$

$$1 \leftrightarrow 0$$

- Example: Given the expression

$$a + (b.c) = (a+b).(a+c)$$

then its dual expression is

$$a . (b+c) = (a.b) + (a.c)$$

Complementing a function


1. Take dual of the function
2. Complement each literals

Example: $F1 = x'yz' + x'y'z$


1. Dual of the function $F1$ is $(x' + y + z')(x' + y' + z)$
2. Complement each literal = $(x + y' + z)(x + y + z')$
Therefore, $F1' = (x + y' + z)(x + y + z')$

Using NAND to represent NOT, OR & AND Gate:


NOT
Gate

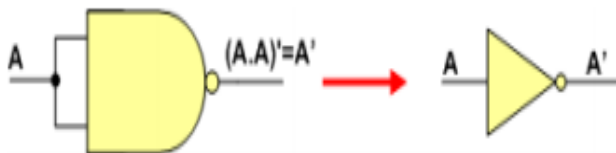

OR
Gate

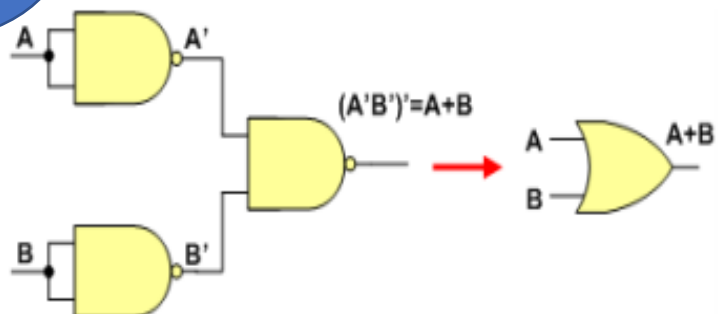


AND
Gate

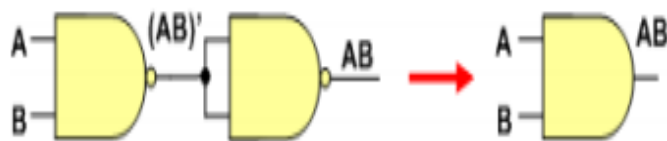


Using NOR to represent NOT, OR & AND Gate:

NOT
Gate

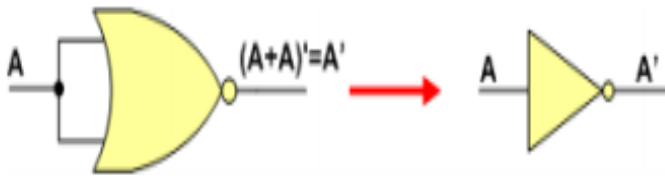

OR
Gate

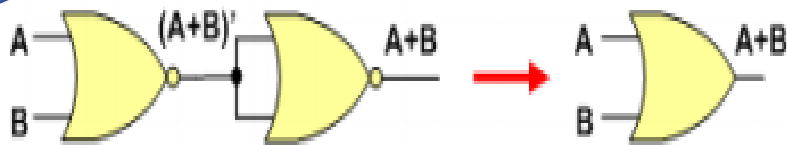

AND
Gate

