

# CSE 260 Lab Assignment 1

NAME: ANIKA ISLAM

ID: 21101298

SECTION: 6

# LAB ASSIGNMENT 1

Report:

(1) Name of the Experiment :

Familiarization of Fundamental Logic Gates


(2) Objective:

- To get familiarised with fundamental logic gates and demonstrates the input output relationships of 2-input AND, OR and NOT gates by constructing their truth tables.
- To get familiarized with other logic gates with like NAND, NOR, XNOR and XOR

(3) Required components and Equipments :

- LOGICSTATE
- LED - BLUE
- LED - GREEN
- LED - PINK
- LED - RED
- LED - YELLOW
- LED - ORANGE
- LED - PURPLE
- AND
- OR
- NOT
- NAND
- XOR

# Experiment Setup

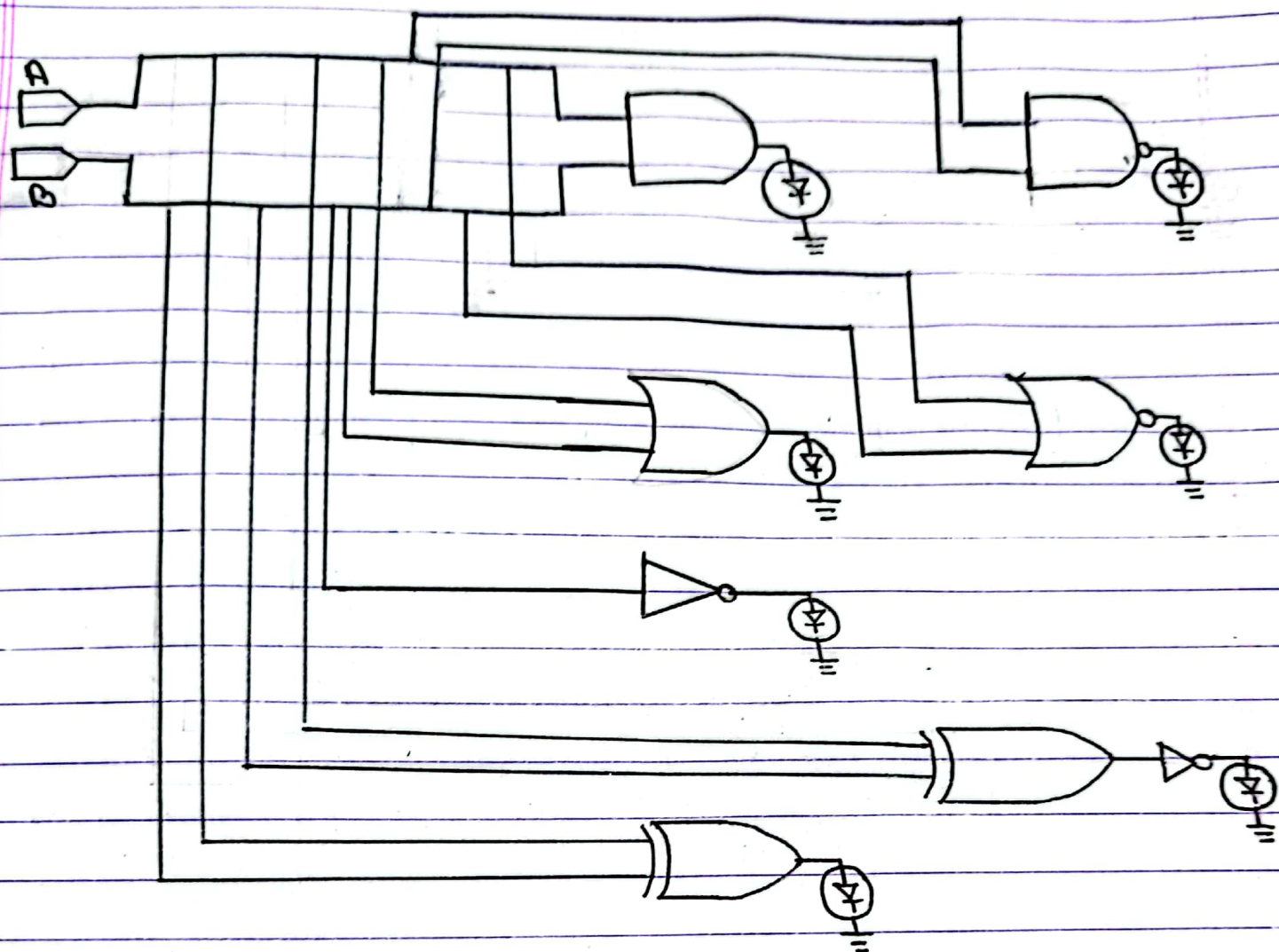



## (b) Results (Truth Table) and Discussions

### • Truth Tables

#### • For AND:

Input		Output
A	B	$A \cdot B$
0	0	0
0	1	0
1	0	0
1	1	1

#### • For NAND:

Input		Output
A	B	$(A \cdot B)'$
0	0	1
0	1	1
1	0	1
1	1	0

#### • For OR:

Input		Output
A	B	$A + B$
0	0	0
0	1	1
1	0	1
1	1	1

#### • For NOR:

Input		Output
A	B	$(A + B)'$
0	0	1
0	1	0
1	0	0
1	1	0

#### • For ~~XOR~~ XOR

Input		Output
A	B	$A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

#### • For NXOR

Input		Output
A	B	$A \odot B$
0	0	1
0	1	0
1	0	0
1	1	1

#### • For NOT

Input	Output
A	$A'$
0	1
1	0

## Discussion:

Difficulty faced: If any of the wire is not placed properly or is loose, then there is a chance of wrong output. For this reason, the whole circuit needs to be set again from the very start. Also, ~~like~~ there is no XOR gate unlike the other gates. So, connecting XOR and NOT be properly needs to be taken into extra caution.

Learnings: The concept of logic gates is more improvised and the ~~use~~ <sup>output</sup> of the logic gates in a circuit is visible in ~~pre~~ through the use of LED/logic probe in the output.

input	output
(AND)	
1	0
0	1
0	0
0	1

input	output
(OR)	
0	0
1	0
0	1
0	1

input	output
(NOT)	
1	0
0	1